


# Section 8.2: Logic Networks

April 15, 2021
 
## Abstract

We examine the relationship between the abstract structure of a Boolean algebra and the practical problem of creating (optimal!) logic networks for solving problems. There is a fundamental equivalence between Truth Functions, Boolean Expressions, and Logic Networks which allows us to pass from one to the other. While a problem might be easiest formulated in terms of a truth function, we might then recast it as a Boolean expression to then feed into a logic network. Then Boolean algebra provides us with a simple mechanism by which to simplify the expressions, and hence to simplify the underlying logic network.

We'll examine the binary adder (and half-adder) as a particular example, which will later be implemented as a Finite State Machine.



$$L = f(s_1, s_2)$$

| $s_1$ | $s_2$ | $L$ |
|-------|-------|-----|
| on    | on    | on  |
| off   | on    | off |
| on    | off   | off |
| off   | off   | on  |

## 1 An Example Application, and Fundamental Parallels

### Example: Two light switches, one light!

The problem is as follows: A light at the bottom of some stairs is controlled by two light switches, one at each end of the stairs. The two switches should be able to control the light **independently**. How do we wire the light?

- A Truth Function:  $f(s_1, s_2) = L$

| $s_1$ | $s_2$ | $L$ |
|-------|-------|-----|
| 1     | 1     | 1   |
| 0     | 1     | 0   |
| 1     | 0     | 0   |
| 0     | 0     | 1   |

As a "Truth function"

- A Boolean Expression (find two equivalent Boolean expressions)

①  $s_1 \cdot s_2 + s_1' \cdot s_2' = f(s_1, s_2)$

$(s_1 \wedge s_2) \vee (s_1' \wedge s_2')$  ✓

②  $s_1 \cdot s_2 + (s_1 + s_2) = f(s_1, s_2)$

As a Boolean Expression




one fewer operations!  
Simplified f.

- A Logic Network (Basic Components, Mechanics, and Conventions)


- Input or output lines are not tied together except by passing through gates:

- OR gate
- AND gate

As a logic network

  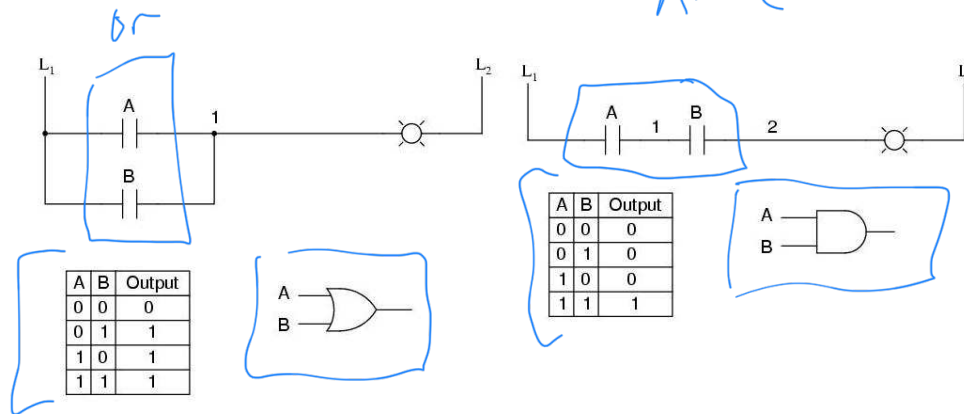

- NOT gate

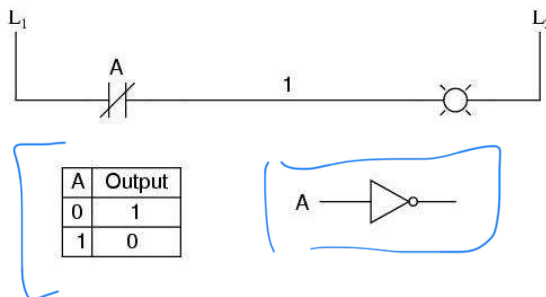

- Lines can be split to serve as input to more than one device.



- There are no loops, with output of a gate serving as input to the same gate. (feedback).
- There are no delay elements.

Figure 8.6, p. 638, shows how to wire an “or” – we do it in parallel (“and” is wired in series).

## 2 Applications

### 2.1 Converting Truth Tables to Boolean Expressions (Canonical Sum-of-Products Form)

Example: Practice 11, p. 645

| $x_1$ | $x_2$ | $x_3$ | $f(x_1, x_2, x_3)$ |
|-------|-------|-------|--------------------|
| 1     | 1     | 1     | 1                  |
| 1     | 1     | 0     | 0                  |
| 1     | 0     | 1     | 1                  |
| 1     | 0     | 0     | 1                  |
| 0     | 1     | 1     | 0                  |
| 0     | 1     | 0     | 0                  |
| 0     | 0     | 1     | 1                  |
| 0     | 0     | 0     | 1                  |

$$x_1 \cdot x_2 \cdot x_3 +$$

$$x_1 \cdot x_2' \cdot x_3 +$$

$$x_1 \cdot x_2' \cdot x_3' +$$

$$x_1' \cdot x_2' \cdot x_3 +$$

$$x_1' \cdot x_2' \cdot x_3' = f(x_1, x_2, x_3)$$

Example: Exercise 15, p. 657

| $x_1$ | $x_2$ | $x_3$ | $f(x_1, x_2, x_3)$ |
|-------|-------|-------|--------------------|
| 1     | 1     | 1     | 0                  |
| 1     | 1     | 0     | 0                  |
| 1     | 0     | 1     | 1                  |
| 1     | 0     | 0     | 1                  |
| 0     | 1     | 1     | 0                  |
| 0     | 1     | 0     | 1                  |
| 0     | 0     | 1     | 0                  |
| 0     | 0     | 0     | 0                  |

$$x_1 \cdot x_2' \cdot x_3 +$$

$$x_1 \cdot x_2' \cdot x_3' +$$

$$x_1' \cdot x_2 \cdot x_3' =$$

$$f(x_1, x_2, x_3) = x_1 \cdot x_2' + x_1' \cdot x_2 \cdot x_3'$$

$$x_1 \cdot x_2' \cdot x_3 + x_1 \cdot x_2' \cdot x_3' + x_1' \cdot x_2 \cdot x_3' =$$


$$x_1 \cdot x_2' (x_3 + x_3') + x_1' \cdot x_2 \cdot x_3' =$$

(notice that you can easily simplify that canonical sum-of-products, using some Boolean algebra.)

### 2.2 Converting Boolean Expressions to Logic Networks

Example: Practice 11, p. 645 (reprise)

Turn that into a logic network ...

 


\* slight modification

Example: Exercise 2, p. 655

$$(x_1 + x_2)' \cdot x_1' \cdot x_3 = f(x_1, x_2, x_3)$$

$$= x_1' \cdot x_2' + x_1' \cdot x_3$$


$$= x_1' \cdot (x_2' + x_3)$$

 

| $x_1$ | $x_2$ | $x_3$ | $f(x_1, x_2, x_3)$ |
|-------|-------|-------|--------------------|
| 1     | 1     | 1     | 0                  |
| 1     | 1     | 0     | 0                  |
| 1     | 0     | 1     | 0                  |
| 1     | 0     | 0     | 0                  |
| 0     | 1     | 1     | 1                  |
| 0     | 1     | 0     | 0                  |
| 0     | 0     | 1     | 1                  |
| 0     | 0     | 0     | 1                  |

## 2.3 Converting Logic Networks to Truth Functions or Boolean Expressions

Example: Exercise 5, p. 655

 

$$x_1 x_2 + x_2' = f(x_1, x_2) = x_1 + x_2'$$

| $x_1$ | $x_2$ | $f(x_1, x_2)$ | $f'(x_1, x_2)$ |
|-------|-------|---------------|----------------|
| 1     | 1     | 1             | 0              |
| 1     | 0     | 1             | 0              |
| 0     | 1     | 0             | 1              |
| 0     | 0     | 1             | 0              |

## 2.4 Simplifying Canonical Form

We can use properties of Boolean algebra to simplify the canonical form, creating a much simpler logic network as a result.

Example: Practice 11, p. 645 (reprise)

$$f(x_1, x_2, x_3) = \begin{matrix} x_1 x_2 x_3 + \\ x_1 x_2 x_3' + x_1 x_2' x_3 + \\ x_1 x_2' x_3' + \\ x_1' x_2 x_3 + \\ x_1' x_2 x_3' + \\ x_1' x_2' x_3 + \\ x_1' x_2' x_3' \end{matrix}$$

$$f(x_1, x_2, x_3) = x_1 x_3 + x_2'$$

$$= x_2' [x_1 x_3 + x_1 x_3' + x_1' x_3 + x_1' x_3']$$

$$= x_2' [x_1 (x_3 + x_3') + x_1' (x_3 + x_3')] = x_2' [x_1 + x_1'] = x_2' \cdot 1 = x_2'$$

$$f'(x_1, x_2) = x_1' x_2$$

$$\therefore f(x_1, x_2) = (x_1' x_2)'$$

$$= x_1 + x_2'$$

Wouldn't it be nice if there were some systematic way of doing this? That's the subject matter of the next section! We'll see two different ways to simplify a canonical sum of products.

## 2.5 An example: Adding Binary numbers

### 2.5.1 Half-Adders

Half-Adder: Adds two binary digits.

$$s = x_1'x_2 + x_1x_2'$$

$$c = x_1x_2$$

$s$  is the result of an "XOR" operation (exclusive or) of the two inputs, whereas  $c$  is the product of the two inputs. Note, however, that the half-adder doesn't implement  $s$  in this way: instead,

$$s = (x_1 + x_2) \cdot (x_1'x_2')' = (x_1 + x_2)(x_1' + x_2')$$

$$= \underbrace{x_1 \cdot x_1'}_0 + x_1x_2' + x_2x_1' + \underbrace{x_2x_2'}_0$$

$$= \underbrace{x_1x_2' + x_2x_1'}_{\text{XOR}}$$

Questions:

a. How?

b. Why? To minimize the logic network


| $x$ | $y$ | $c$ | $s$ |
|-----|-----|-----|-----|
| 0   | 0   | 0   | 0   |
| 0   | 1   | 0   | 1   |
| 1   | 0   | 0   | 1   |
| 1   | 1   | 1   | 0   |

Canonical sum of products

$s$  is an "exclusive or" XOR

binary sum

The "Half-adder":

 


### 2.5.2 Full-Adders

$s$  is simpler; & we reuse the computation of  $c_i$

Full-Adder: Adds two digits plus the carry digit from the preceding step (which we can create out of two half-adders!).

- Given the preceding carry digit  $c_{i-1}$ , and binary digits  $x_i$  and  $y_i$ .
- We'll use a half-adder to add  $x_i$  to  $y_i$ , obtaining write digit  $\sigma$  and carry digit  $\gamma$ .
- Then use a half-adder to add the carry digit  $c_{i-1}$  to  $\sigma$ ; the write digit is  $s_i$ , and call the carry digit  $c$ .
- To get the carry digit  $c_i$ , compare the carry digits  $c$  and  $\gamma$ : if either gives a 1, then  $c_i = 1$  (so it's an "or").

 

$$s_i = c_{i-1}'x_i'y_i + c_{i-1}'x_iy_i' + c_{i-1}x_i'y_i' + c_{i-1}x_iy_i$$

Let's derive all that from the truth functions, representing the sum from the full-adder:

| $c_{i-1}$ | $x_i$ | $y_i$ | $c_i$ | $s_i$ |
|-----------|-------|-------|-------|-------|
| 0         | 0     | 0     | 0     | 0     |
| 0         | 0     | 1     | 0     | 1     |
| 0         | 1     | 0     | 0     | 1     |
| 0         | 1     | 1     | 1     | 0     |
| 1         | 0     | 0     | 0     | 1     |
| 1         | 0     | 1     | 1     | 0     |
| 1         | 1     | 0     | 1     | 0     |
| 1         | 1     | 1     | 1     | 1     |

$$c_i(c_{i-1}, x_i, y_i) = c_{i-1}'x_i'y_i + c_{i-1}'x_iy_i' + c_{i-1}x_i'y_i' + c_{i-1}x_iy_i$$

Canonical sum of products

Note:  $x_i'y_i' + x_iy_i = (x_i'y_i + x_iy_i)'$

So the canonical sum of products forms of each function are

$$\begin{aligned}
 s_i(c_{i-1}, x_i, y_i) &= c_{i-1}'x_i'y_i + c_{i-1}'x_iy_i' + c_{i-1}x_i'y_i' + c_{i-1}x_iy_i \\
 &= c_{i-1}'(x_i'y_i + x_iy_i') + c_{i-1}(x_i'y_i' + x_iy_i)
 \end{aligned}$$

Define  
 $\sigma \equiv x_i'y_i + x_iy_i'$   
 $\gamma \equiv x_i'y_i' + x_iy_i$   
 The output of a half-adder

and

$$s_i = c_{i-1}'\sigma + c_{i-1}\gamma$$

← The write digit of a half-adder!

$$\begin{aligned}
 c_i(c_{i-1}, x_i, y_i) &= c_{i-1}'x_iy_i + c_{i-1}x_i'y_i + c_{i-1}x_iy_i' + c_{i-1}x_iy_i \\
 &= x_iy_i + c_{i-1}(x_i'y_i + x_iy_i') = \gamma + c_{i-1}\sigma = \gamma + c
 \end{aligned}$$

We recognize these quantities in terms of half-adders:

- We recognize the write digit  $\sigma$  and the carry digit  $\gamma$  of the half-adder of  $x_i$  and  $y_i$ .
- Then  $s_i$  is just the write digit  $s$  of the half-adder of  $c_{i-1}$  and  $\sigma$ ;
- Meanwhile,  $c_i$  is the sum of  $\gamma$  and the carry digit  $c$  of the half-adder of  $c_{i-1}$  and  $\sigma$ .
- That is illustrated in this figure:

The carry digit of the same half-adder

"Black Box" is Full Binary Adder


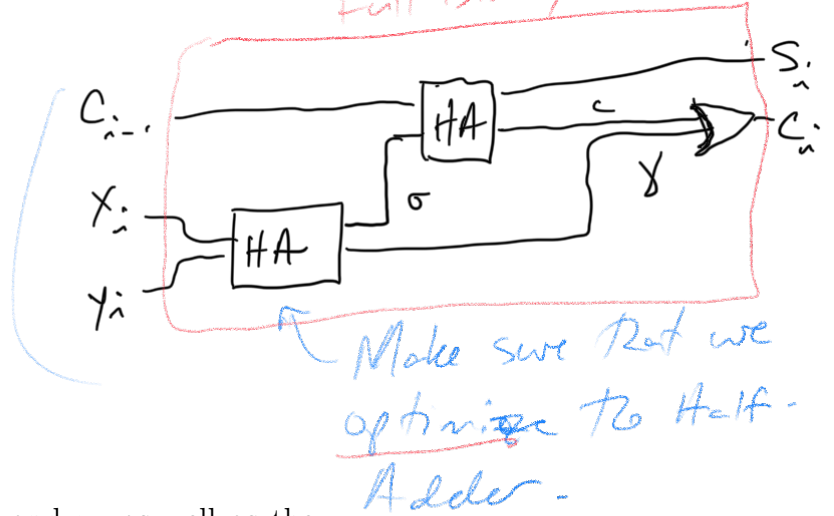


Figure 1: The full-adder takes input digits  $x_i$  and  $y_i$ , as well as the carry digit  $c_{i-1}$  from the previous step and computes write digit  $s_i$  and carry digit  $c_i$ . Then do it again!

Example: Practice 12, p. 650

 